

b) Rules for Multiple Variables

10) Changing Rule (commutative)

$$X + Y = Y + X$$

$$X \cdot Y = Y \cdot X$$

11) Union Rule

$$X + (Y + Z) = (X + Y) + Z = X + Y + Z$$

$$X(YZ) = (XY)Z = XYZ$$

12) Distribution Rule

$$X(Y + Z) = XY + XZ$$

$$X + (YZ) = (X + Y) \cdot (X + Z)$$

13) Absorption Rule

$$X + XY = X$$

$$X \cdot (X + Y) = X$$

14) De Morgan Rule

$$\overline{(X + Y)} = \bar{X} \cdot \bar{Y}$$

$$\overline{(X \cdot Y)} = \bar{X} + \bar{Y}$$

15) $X + \bar{X}Y = X + Y$

This rules can be proven by giving 0 or 1 values to the variables.

Samples

1) $X = ACD + \bar{A}BCD$

will be simplified.

$$= CD(A + \bar{A}B)$$

15. rule

$$A + \bar{A}B \rightarrow A + B$$

$$= CD(A + B)$$

$$= ACD + BCD$$

2) $Y = ABC + AB\bar{C}$

$$= AB(C + \bar{C})$$

Distribution Rule

$$= AB.1$$

$$= AB$$

3) $Y = \overline{(\bar{A} + C)(B + \bar{D})} + AC$

$$= \overline{(\bar{A} + C)} + \overline{(B + \bar{D})} + AC$$

De Morgan

$$= \bar{\bar{A}}\bar{C} + \bar{B}\bar{\bar{D}} + AC$$

De Morgan


$$= A\bar{C} + \bar{B}D + AC$$

$$= A(\bar{C} + C) + \bar{B}D$$

Distribution

$$= A.1 + \bar{B}D$$

$$= A + \bar{B}D$$

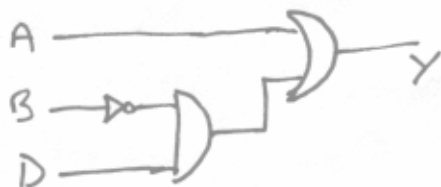

NOT-AND, NOT-OR GATES



instead of following gates of
AND, OR and NOT gates.

instead of using two different gates
use single special gate
NOT-AND NOT-OR

Examples



1)

A	B	AB	\overline{AB}
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

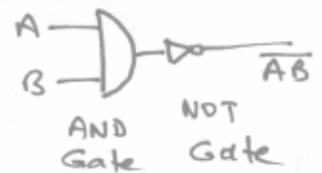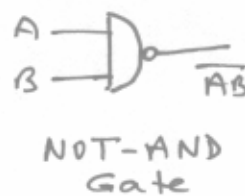


2)

A	B	A+B	$\overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

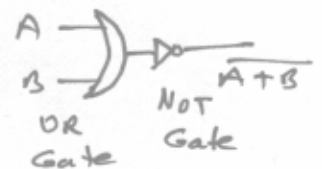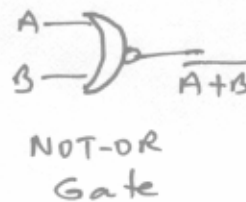

3)

$$X = \overline{AB} + (\overline{C+D})$$

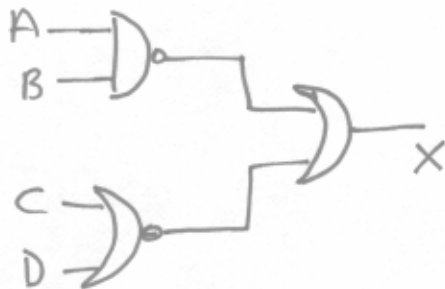

BOOLEAN FUNCTIONS AND LOGICAL DESIGN

To handle a Boolean function:

- 1) Prepare a truth table for variables
- 2) Decide to which cases will be 1 in logically, make it AND operation
- 3) If there are more than one AND operation, collect them in OR operation
(Addition of multiplications)
- 4) Simplify the equation in 3.
- 5) Draw the logical circuit.

Example

1)

A	B	C
0	0	0
0	1	1
1	0	0
1	1	0

$\rightarrow C = \bar{A}B$

2)

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

$\rightarrow \bar{A}B$
 $\rightarrow A\bar{B}$

$C = \bar{A}B + A\bar{B}$

3)

A	B	C	Y
0	0	0	0
0	0	1	1 $\rightarrow \bar{A}\bar{B}C$
0	1	0	0
0	1	1	1 $\rightarrow \bar{A}BC$
1	0	0	0
1	0	1	1 $\rightarrow A\bar{B}C$
1	1	0	0
1	1	1	0

$$Y = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C \quad (\text{Addition of multiplication})$$

$$= C(\bar{A}\bar{B} + \bar{A}B + A\bar{B})$$


$$= C(\bar{A}\bar{B} + \bar{A}\bar{B} + \bar{A}B + A\bar{B}) \quad (\text{if we suppose } AB = X,$$

$$= C(\bar{A}(B + \bar{B}) + \bar{B}(\bar{A} + A))$$

$$= C(\bar{A} \cdot 1 + \bar{B} \cdot 1)$$

$$= C(\bar{A} + \bar{B})$$

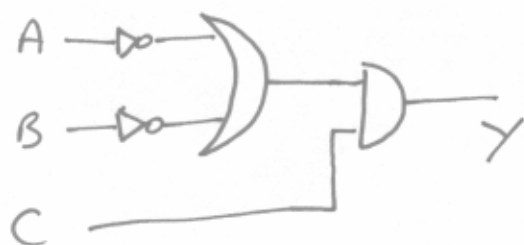$X + X = X$
So, adding $\bar{A}\bar{B}$
will not change
the result.



Question

An alarm system will be prepared to a house. The house has a door and a window.



Door is closed 0
 " " open 1
 Window is closed 0
 " " open 1
 Button is pressed 1
 " is not pressed 0

There is a button near the door.
 If this button is pressed first, and later door or window is open, alarm will not work. Other cases alarm works.

D	W	B	A
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$\bar{D}W\bar{B}$ (Button is not pressed but the door is open)

$D\bar{W}\bar{B}$

$DW\bar{B}$

$$\begin{aligned}
 A &= \bar{D}W\bar{B} + D\bar{W}\bar{B} + DW\bar{B} \\
 &= \bar{B}(\bar{D}W + D\bar{W} + DW) \\
 &= \bar{B}(\bar{D}W + D\bar{W} + DW + DW) \\
 &= \bar{B}(W(\bar{D} + D) + D(\bar{W} + W)) \\
 &= \bar{B}(W + D)
 \end{aligned}$$

